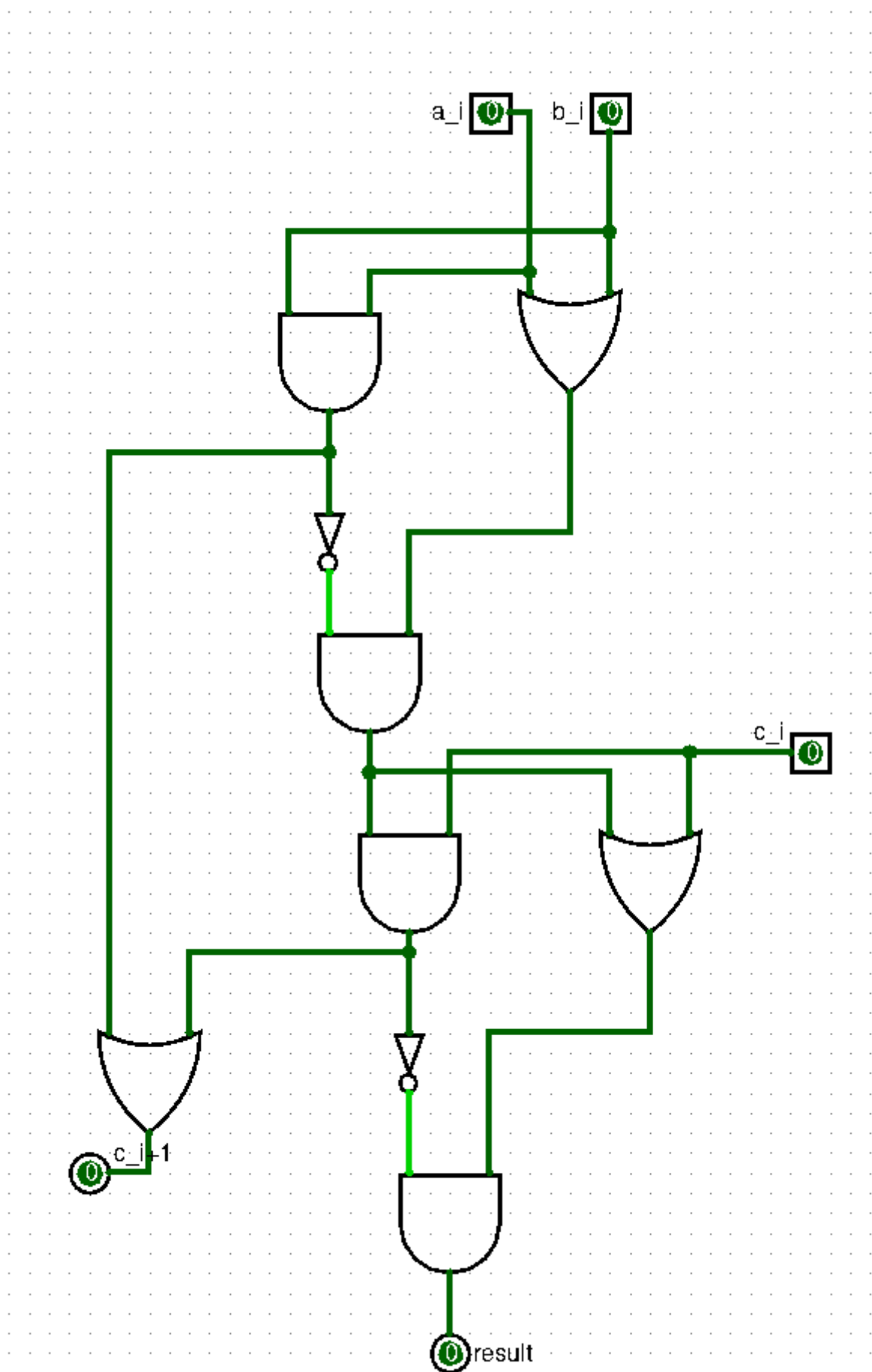


# CSE-331 Homework 3 Report


|                         |                        |         |
|-------------------------|------------------------|---------|
| ☰ Computer Organization | HomeWork               | Lecture |
| 📅 Created               | @Dec 20, 2020          |         |
| ☰ Number                | 171044036              |         |
| 👤 Property              | 👤 Baran Hasan Bozduman |         |

In this project i designed adder shifter by myself it also works for overflowed numbers. I can start with introduce my components


## 1-Bit Adder



## 32-Bit Adder

 


## Shifter Register

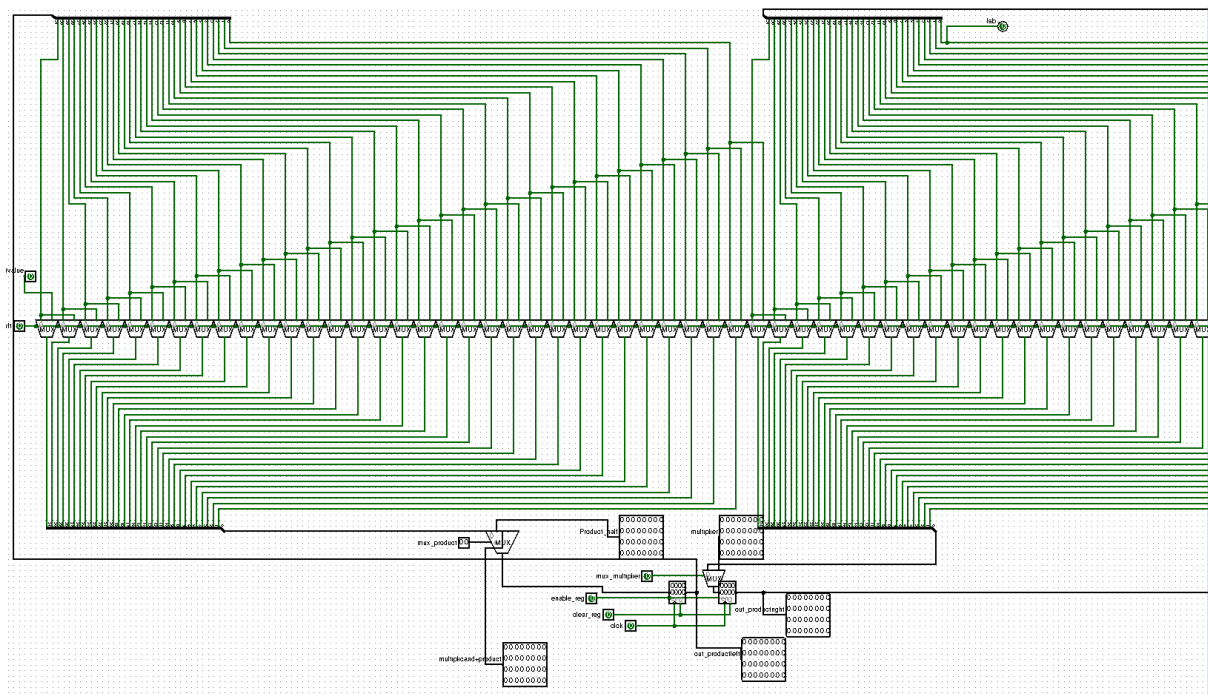


As you see above i designed a shifter with muxes so i can arrange the signals with using control unit i can decide at the current state it will make a shift or not if it will, right shift can be 1 and according to overflow bit i send shift value so we can also do arithmetic shift by deciding muxes when we come to register inputs as default it gets shifted values, and also we use initial values and summation result for left register

## Datapath

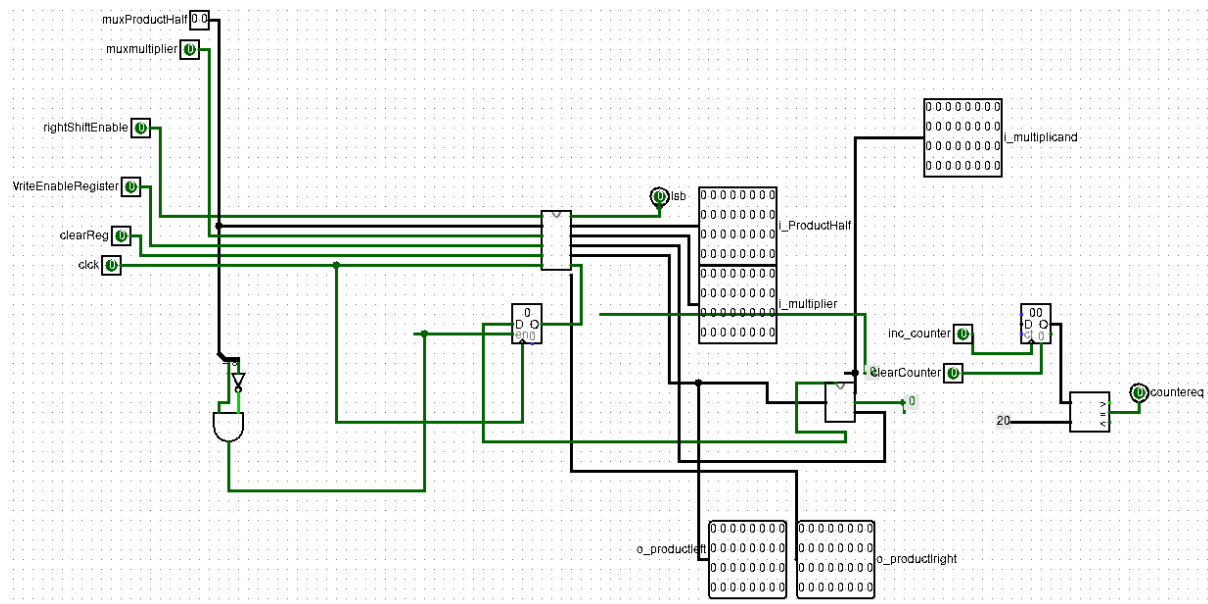


You can see extra register in datapath also for the overflow situations so if to pretend overflow situations i keep the carry out bit in a register so when we make a shift the carry out bit comes beginning of the number

## Control Unit

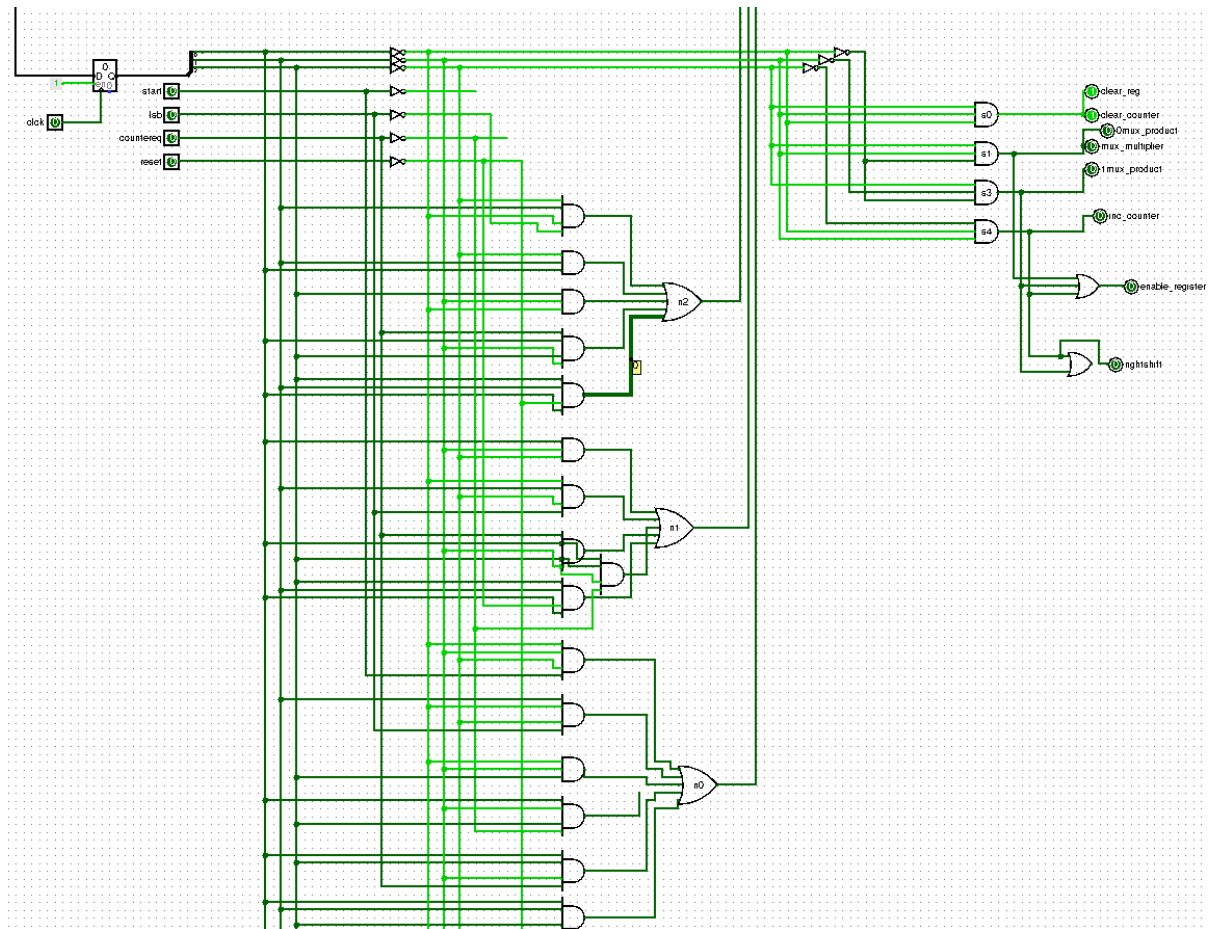

I arranged the signals according to my states

## Finite State Machine And Program Flow

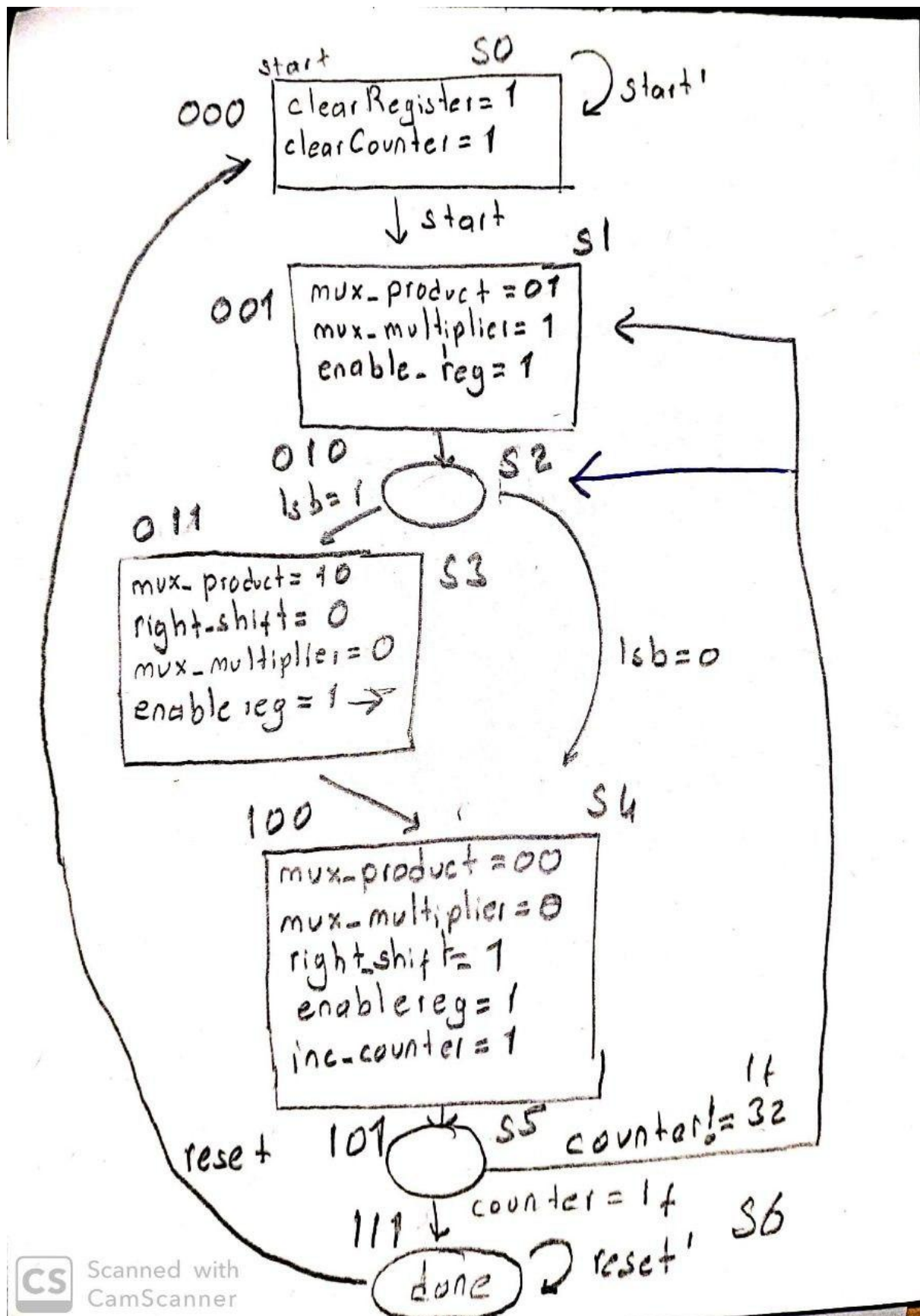

to determine next state here is my truth table below



| Inputs |    |    |       |     |         | Out Puts |    |    |
|--------|----|----|-------|-----|---------|----------|----|----|
| P2     | P1 | P0 | start | lsb | counteq | N2       | N1 | N0 |
| 0      | 0  | 0  | 0     | -   | -       | 0        | 0  | 0  |
| 0      | 0  | 0  | 1     | -   | -       | 0        | 0  | 1  |
| 0      | 0  | 1  | -     | -   | -       | 0        | 1  | 0  |
| 0      | 1  | 0  | -     | 1   | -       | 0        | 1  | 1  |
| 0      | 1  | 0  | -     | 0   | -       | 1        | 0  | 0  |
| 0      | 1  | 1  | -     | -   | -       | 1        | 0  | 0  |
| 1      | 0  | 0  | -     | -   | -       | 1        | 0  | 1  |
| 1      | 0  | 1  | -     | -   | 0       | 0        | 1  | 0  |
| 1      | 0  | 1  | -     | -   | 1       | 1        | 1  | 1  |
| 1      | 1  | 1  | -     | -   | -       | 1        | 1  | 1  |
| 1      | 1  | 1  | -     | -   | -       | 0        | 0  | 0  |

+ reset 0  
→ reset 1

$$N2 = P2'P1P0'lsb' + P2'P1P0 + P2P1'P0' + P2P1'P0counteq + P2P1P0reset'$$

$$N1 = P2'P1'P0 + P2'P1P0'lsb + P2P1'P0counteq + P2P1P0reset' + P2P1'P0counteq'$$

$$N0 = P2'P1'P0'start + P2'P1P0'lsb + P2P1'P0' + P2P1'P0counteq + P2P1P0reset'$$

And to determine signals according to what state are we here my other table


| Inputs |    |    |    |                |               |               |               |                |                 |             |             |  |
|--------|----|----|----|----------------|---------------|---------------|---------------|----------------|-----------------|-------------|-------------|--|
|        | P2 | P1 | P0 | clear register | clear counter | 2 mux product | 1 mux product | mux multiplier | enable register | right shift | inc counter |  |
| S0     | 0  | 0  | 0  | 1              | 1             | 0             | 0             | 0              | 0               | 0           | 0           |  |
| S1     | 0  | 0  | 1  | 0              | 0             | 0             | 1             | 1              | 1               | 0           | 0           |  |
| S2     | 0  | 1  | 0  | 0              | 0             | 0             | 0             | 0              | 0               | 0           | 0           |  |
| S3     | 0  | 1  | 1  | 0              | 0             | 1             | 0             | 0              | 1               | 1           | 0           |  |
| S4     | 1  | 0  | 0  | 0              | 0             | 0             | 0             | 0              | 1               | 1           | 1           |  |
| S5     | 1  | 0  | 1  | 0              | 0             | 0             | 0             | 0              | 0               | 0           | 0           |  |
| S6     | 1  | 1  | 1  | 0              | 0             | 0             | 0             | 0              | 0               | 0           | 0           |  |

✓ clear register = S0  
 ✓ clear counter = S0  
 ✓ 2 mux-product = S3  
 ✓ 1 mux product = S1  
 ✓ mux-multiplier = S1  
 ✓ enable register = S5 + S3 + S4  
 ✓ right shift = S3 + S4  
 ✓ inc-counter = S4


## TESTS

### 1- ONE SIDE ZERO




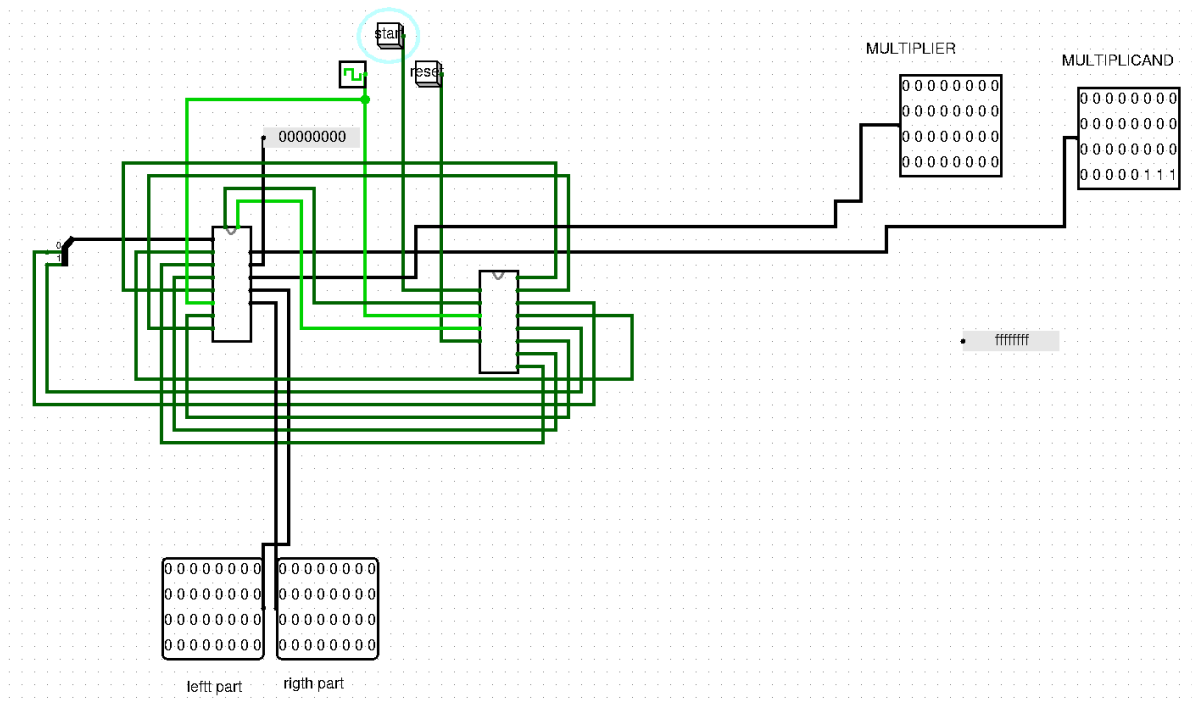


## 2-ONE SIDE 1

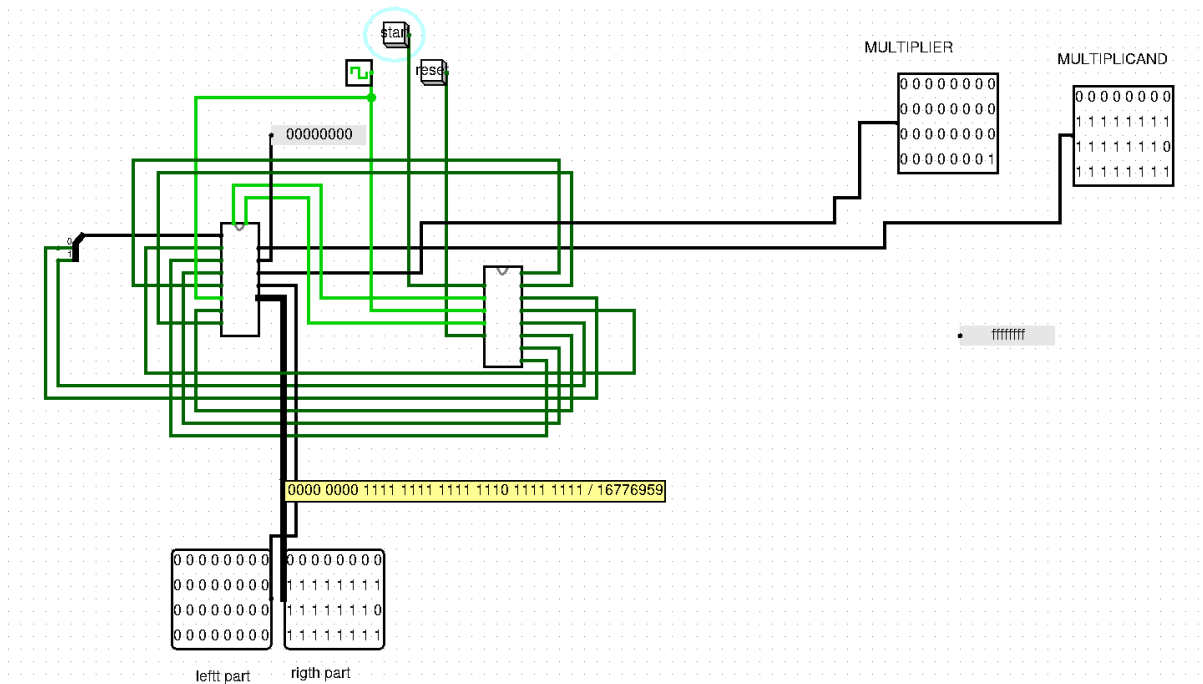


## 3-THERE SOME NUMS BOTH SIDE

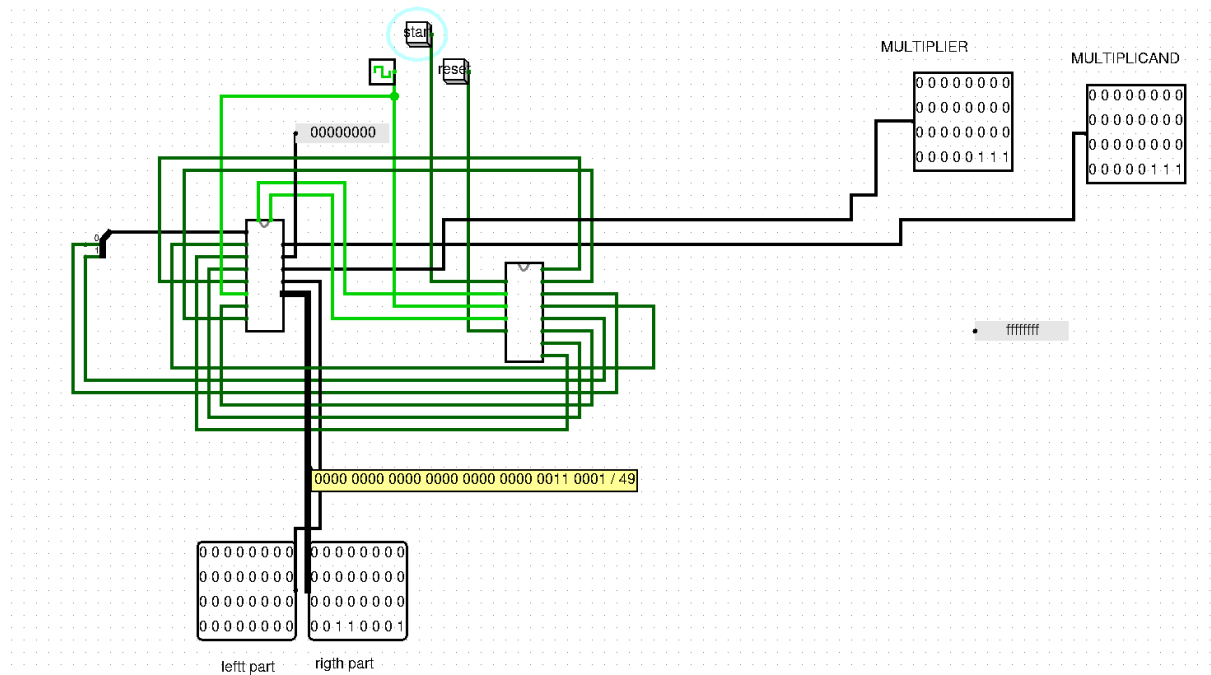

#### 4-TEST CASE

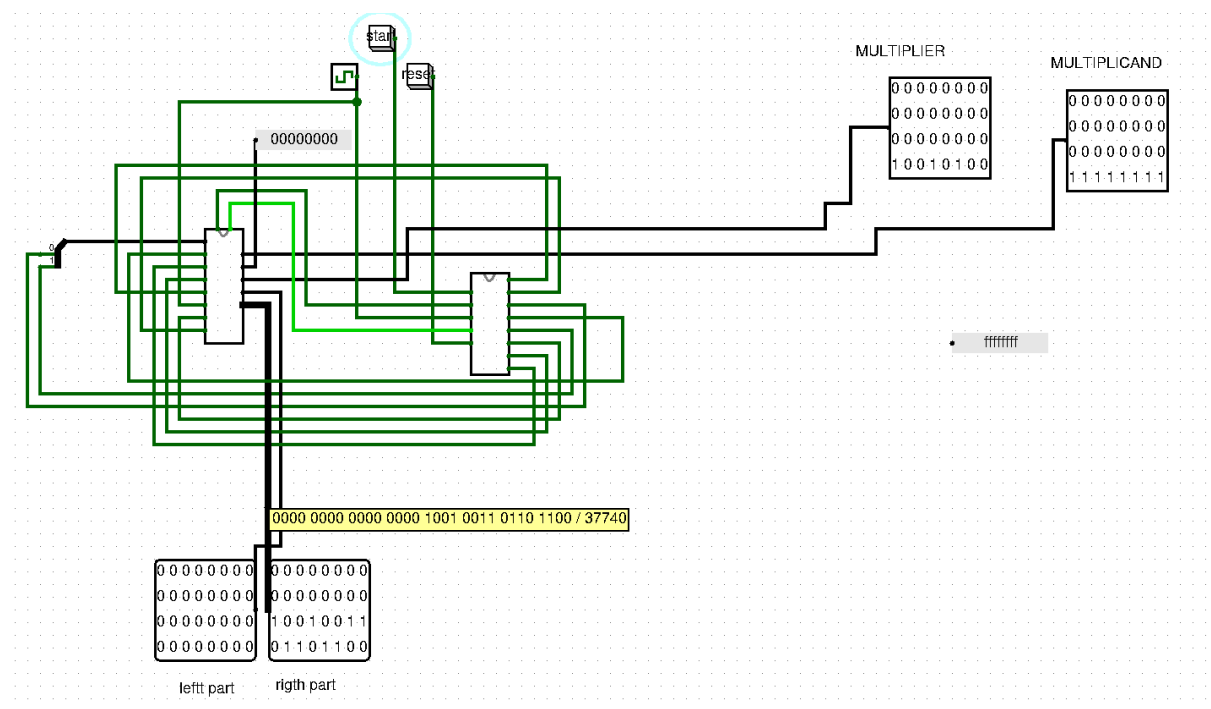

#### 5-TEST CASE

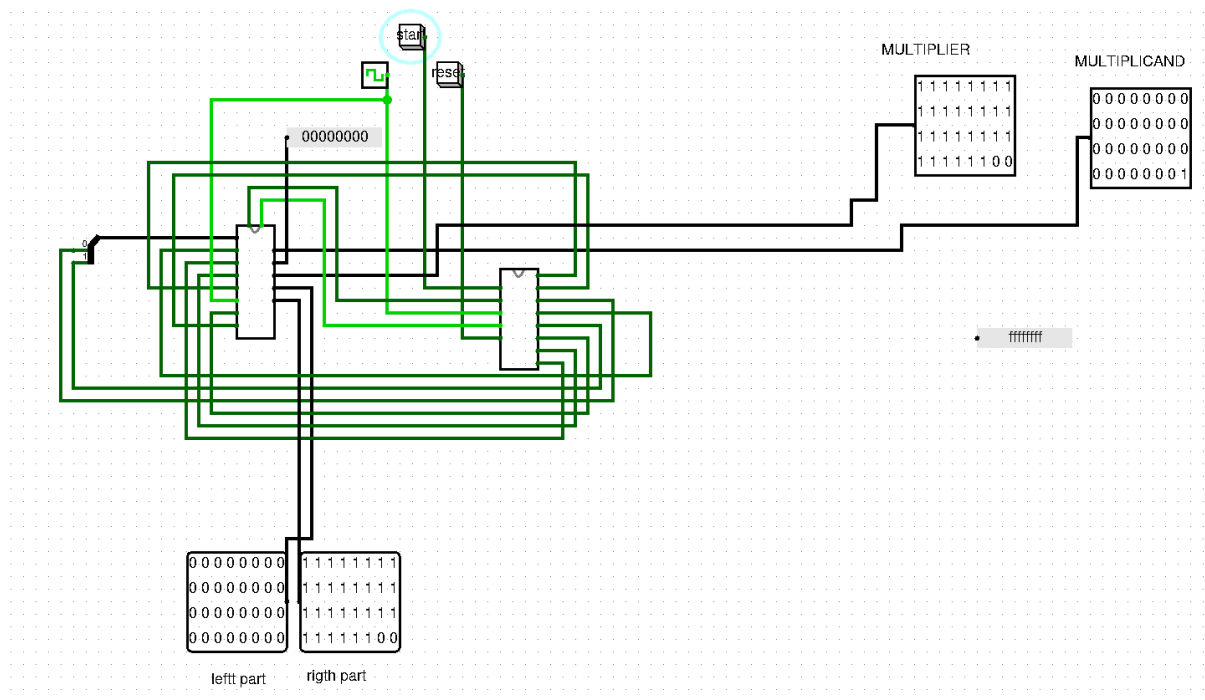

## 6- TEST OVERFLOW

